

دانشگاه فنی حرفه ایی انقلاب اسلامی
دانشکده مهندسی برق



آموزش مجازی درس
مدارهای جریان متناوب

جلسه چهارم
فیلترهای میان گذر


ارائه دهنده: دکتر علیرضا ناطقی

فیلتر میان گذر و میان نگذر


Band Pass Filter and Band Stop Filter

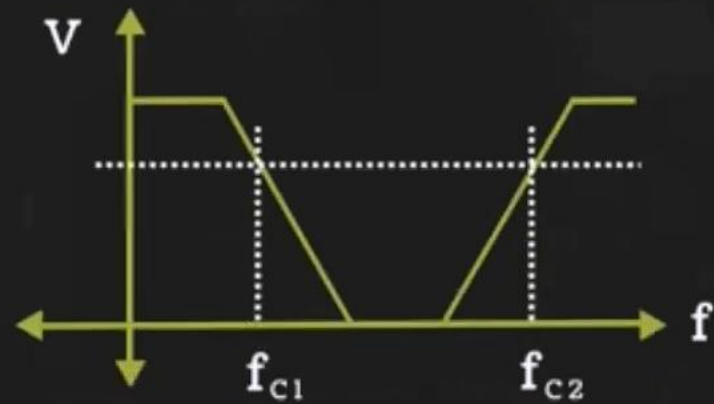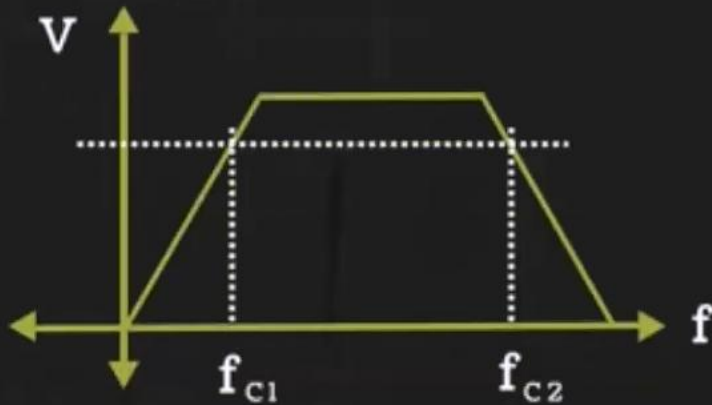

RC Low Pass Filter

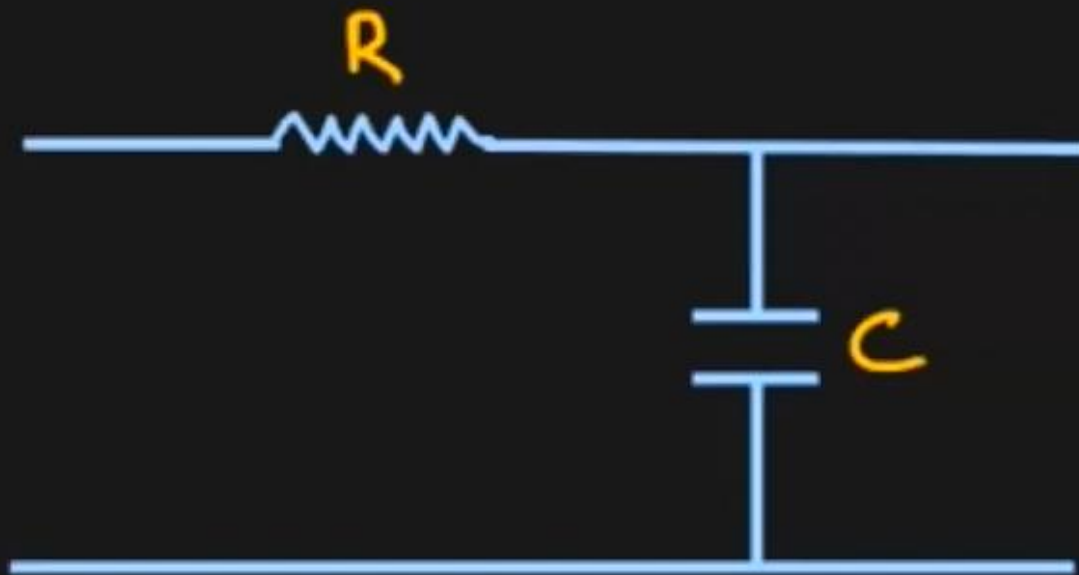

RC High Pass Filter

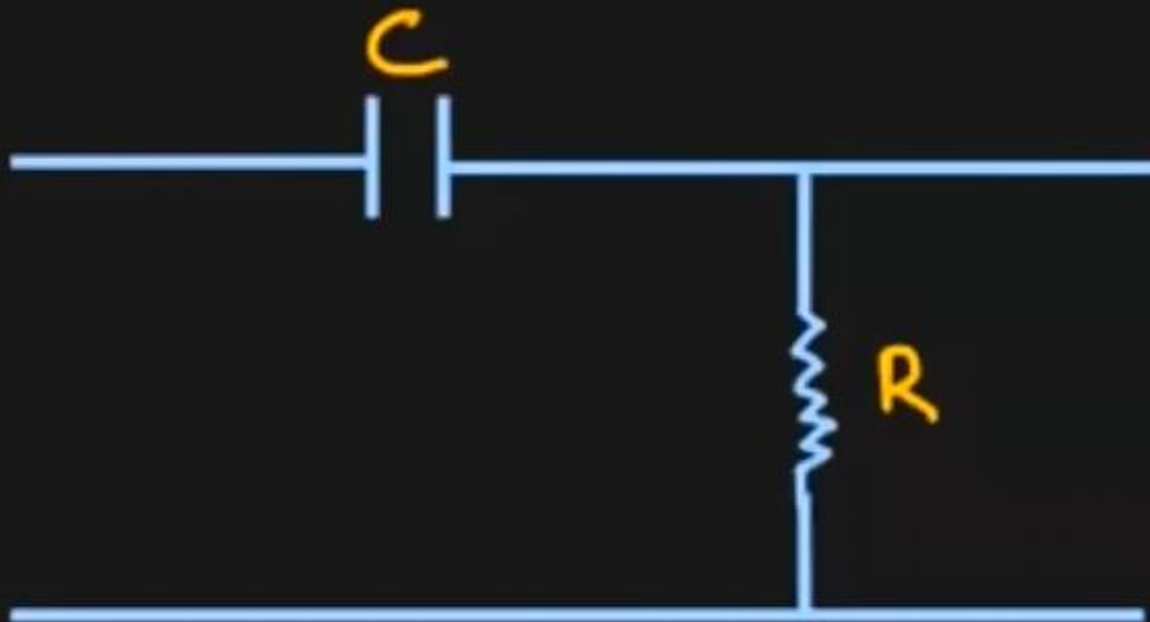

Low Pass Filter




High Pass Filter



Band Pass Filter



Band pass Filter

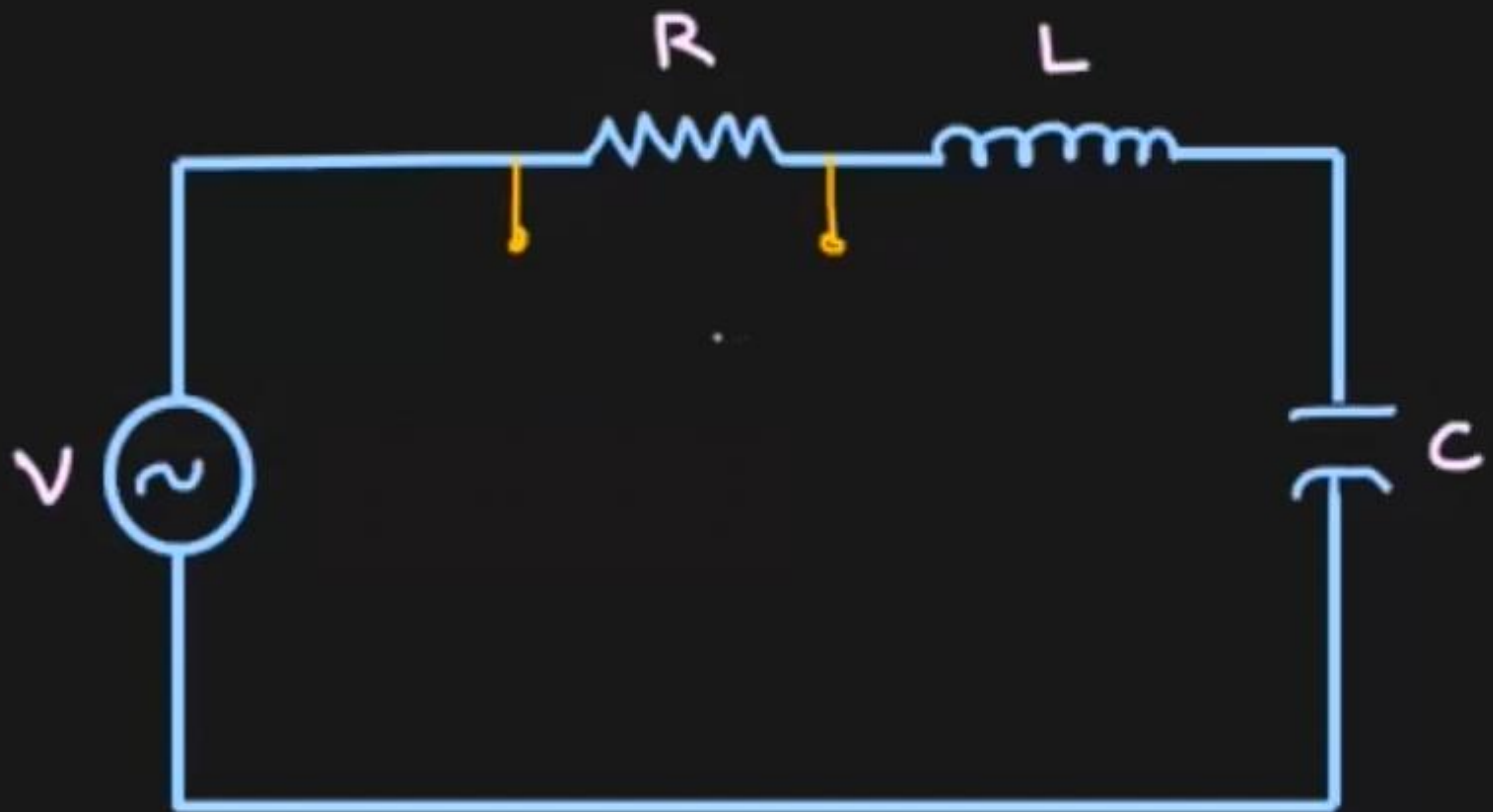


Band Pass Filter

High Pass Filter

Low Pass Filter



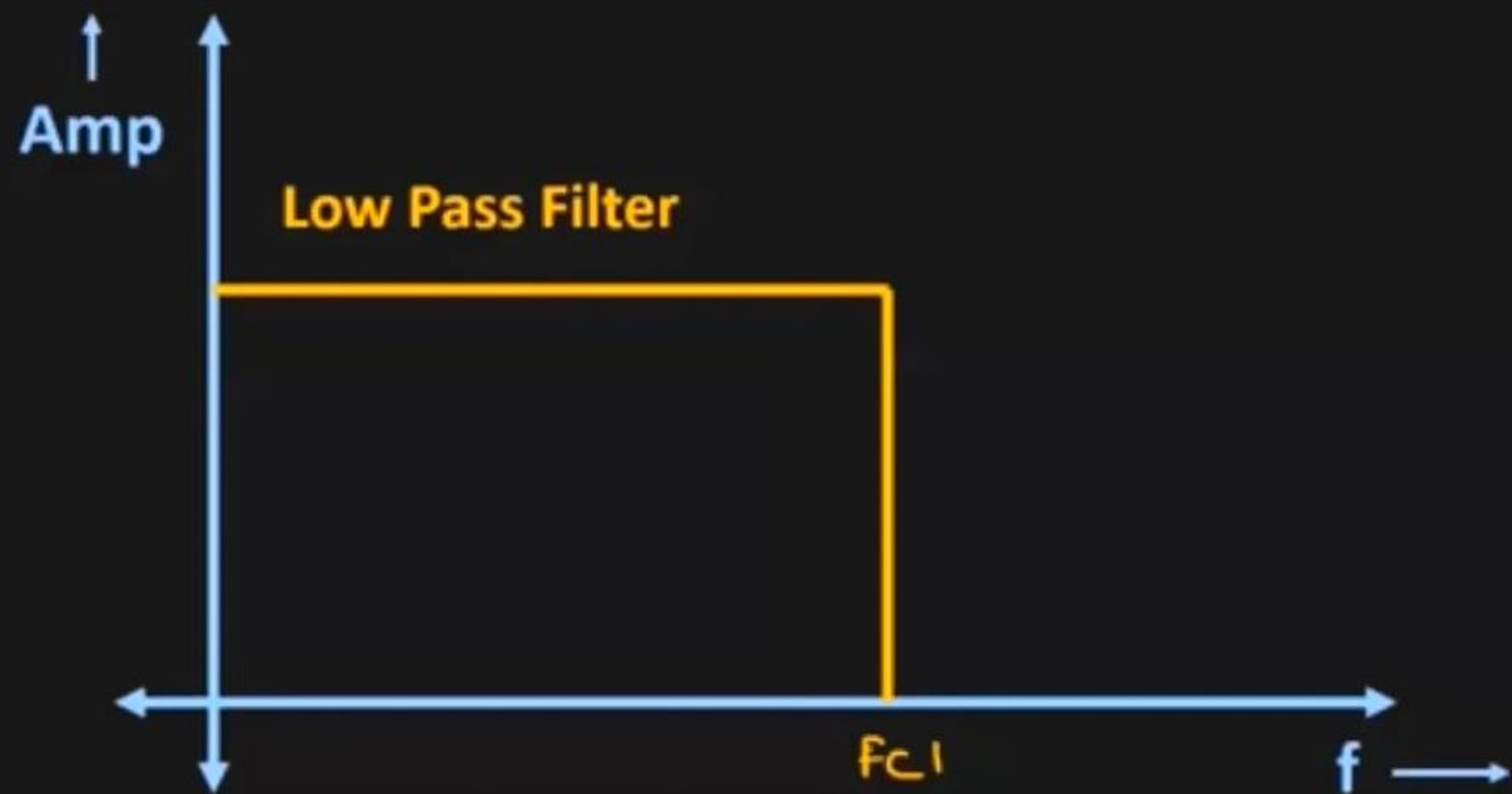


High Pass Filter




Band Pass Filter




Band Pass Filter

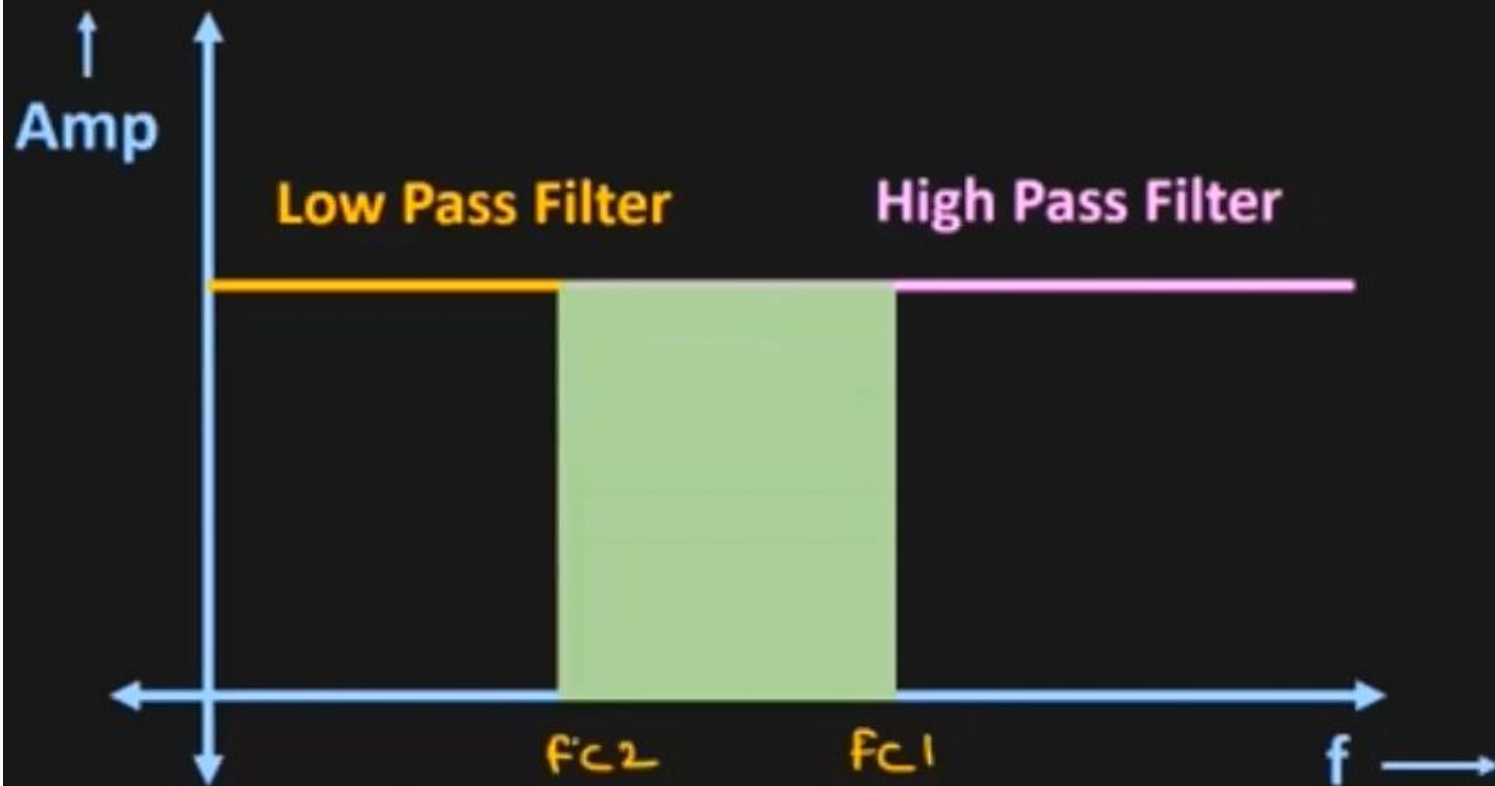


Band Pass Filter

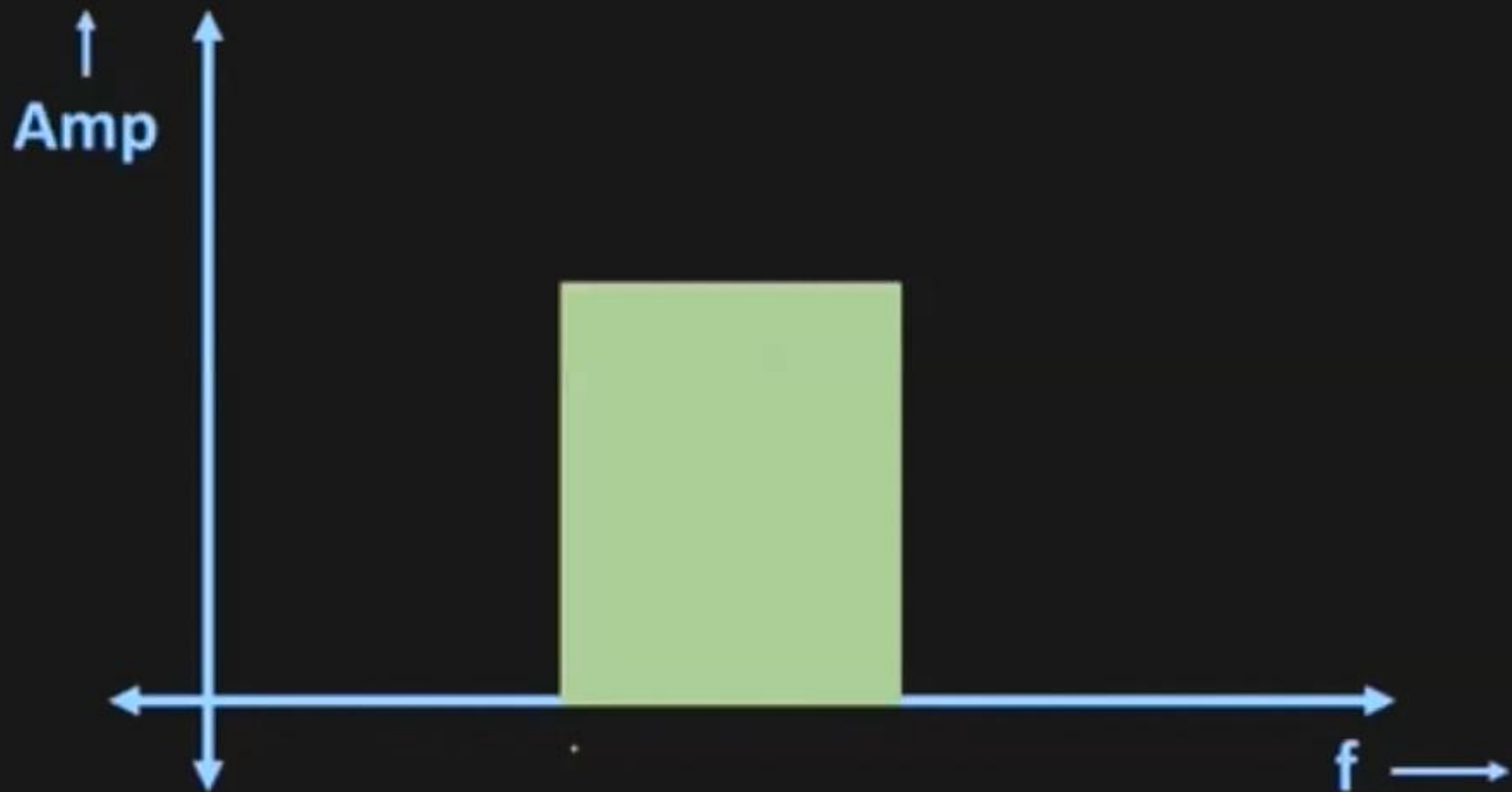

Band Pass Filter

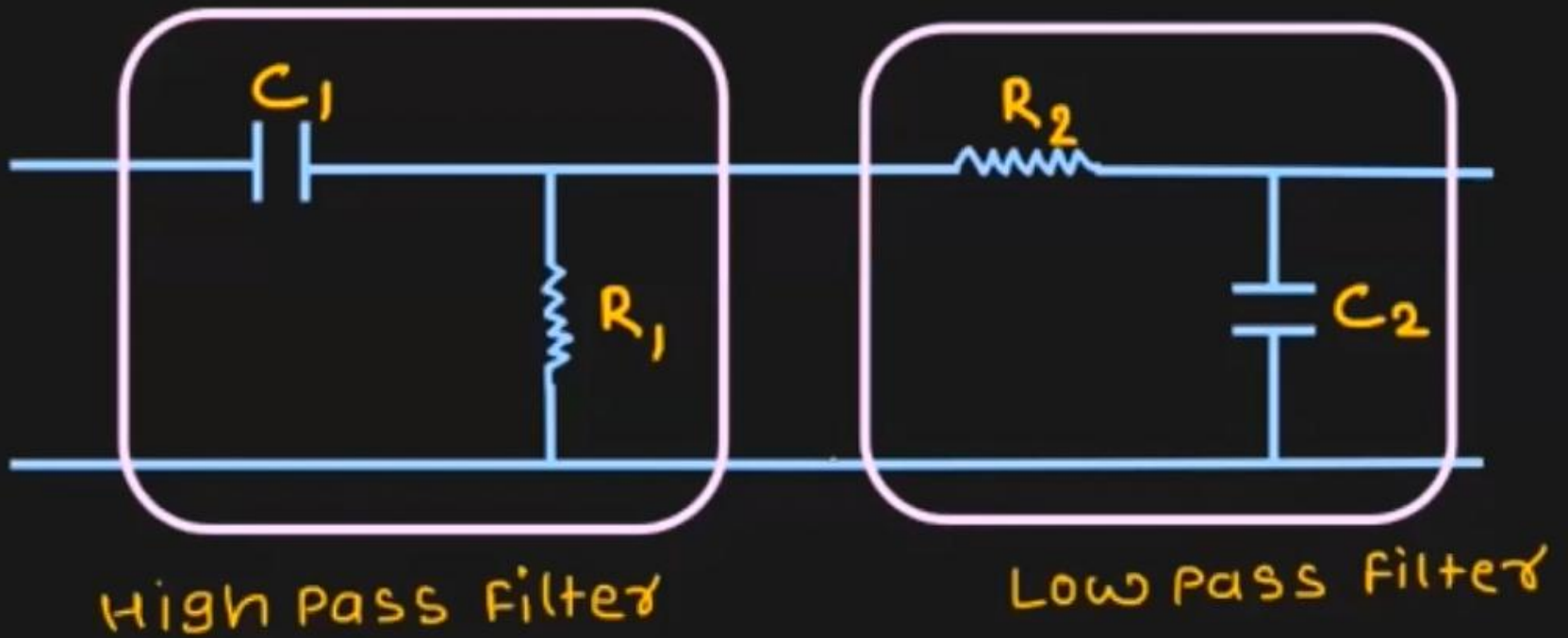

Band Pass Filter

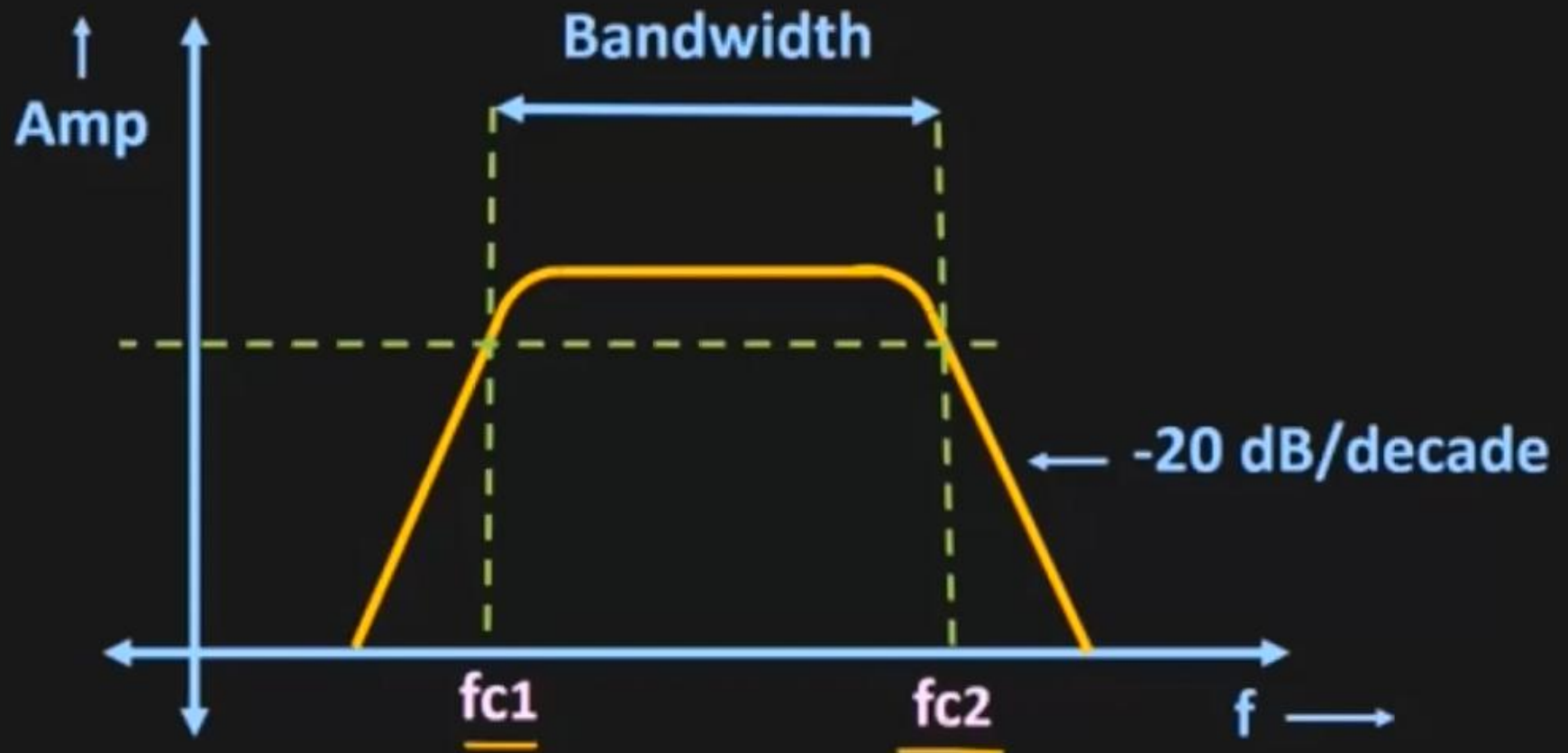


Band pass Filters


$$\text{Bandwidth} = f_{c2} - f_{c1}$$

$$\text{Center Frequency} = \sqrt{f_{c2} * f_{c1}}$$

Band Pass Filter

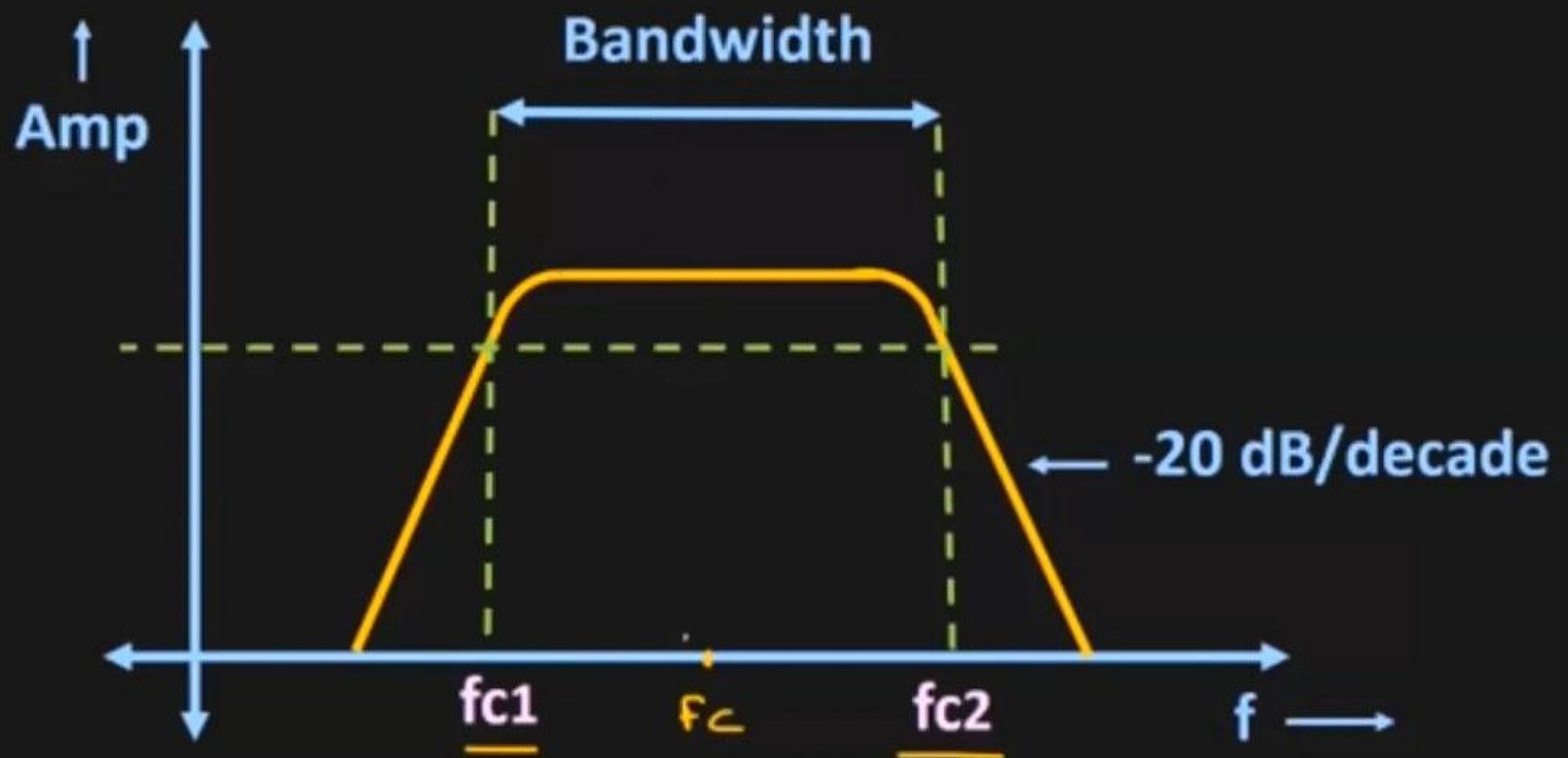


Phase Response

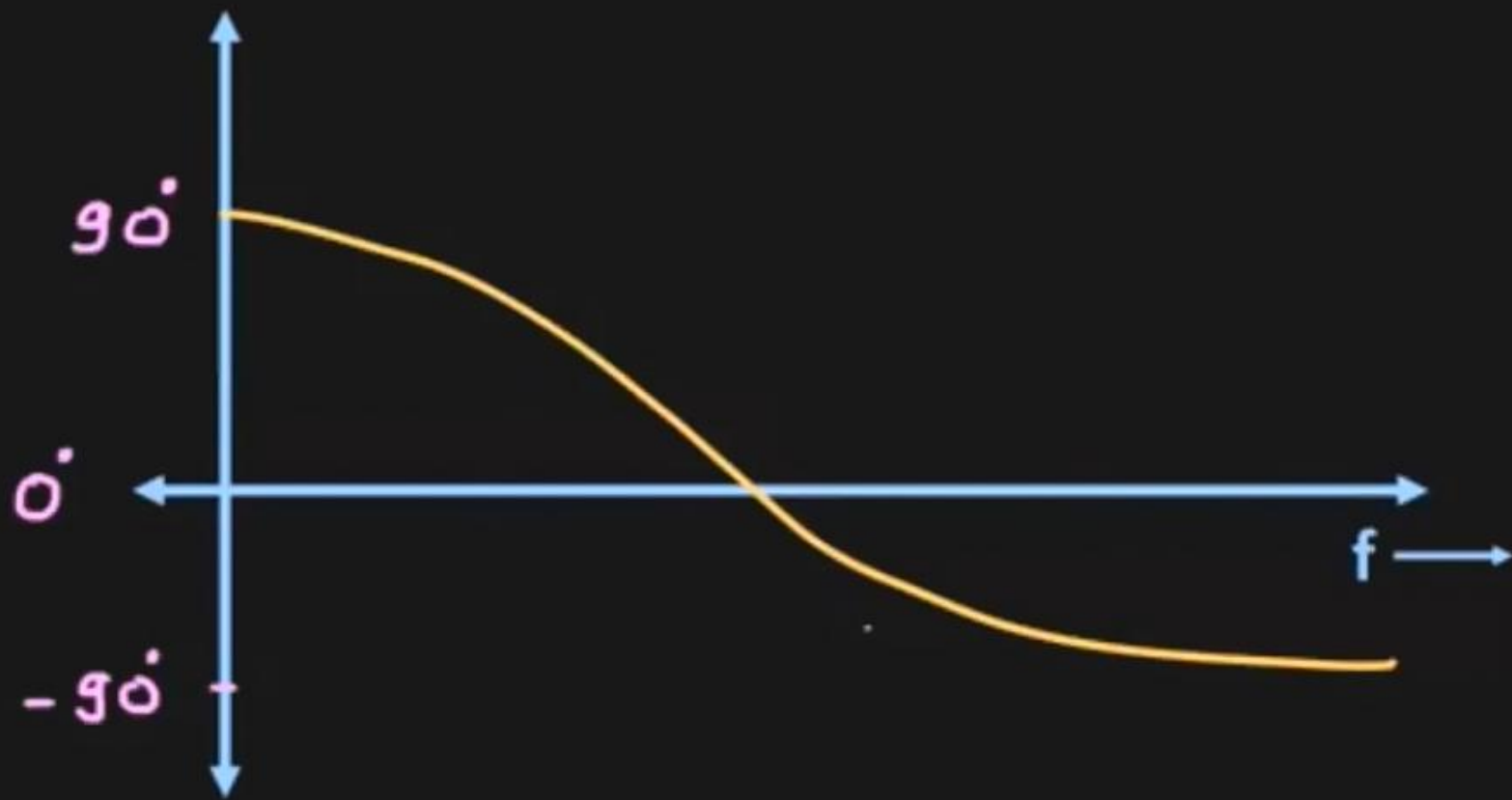

Example

Find the bandwidth of the given Filter

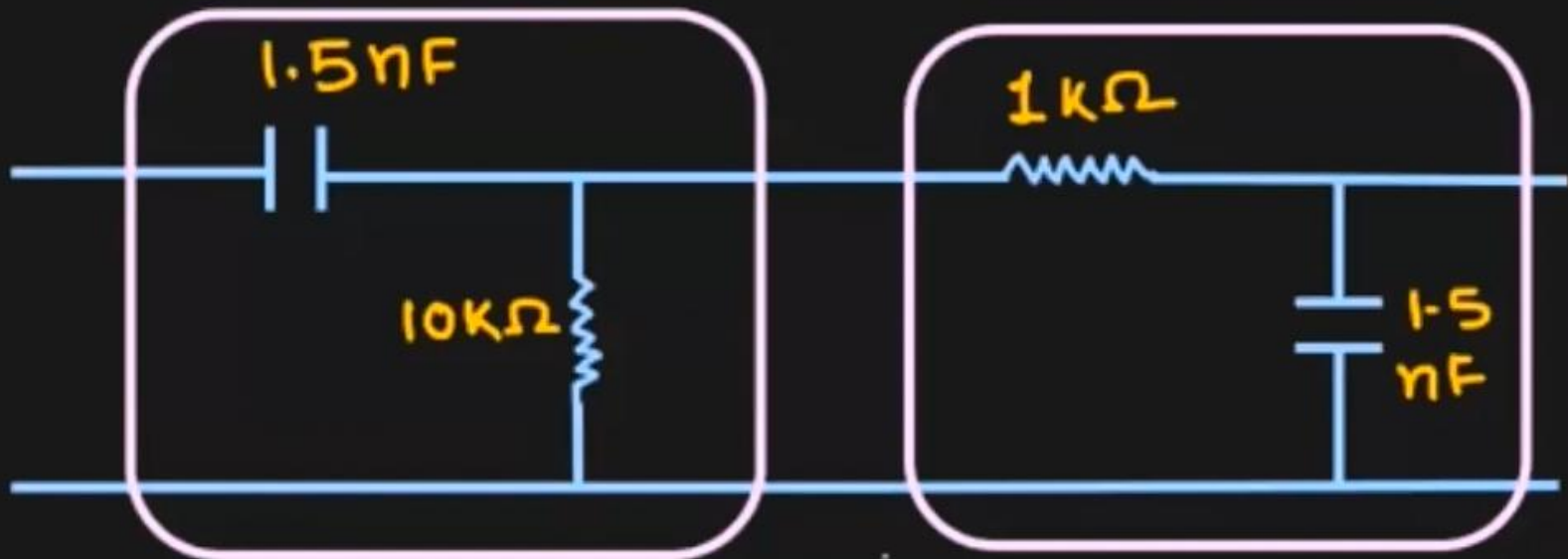

For High Pass Filter:


$$f_{c1} = \frac{1}{2\pi R C} = \frac{1}{2\pi \times (10k) \times (1.5nF)} = 10.61kHz$$

Example

Find the bandwidth of the given Filter

$$f_{c1} = 10.61 \text{ kHz}$$

$$f_{c2}$$

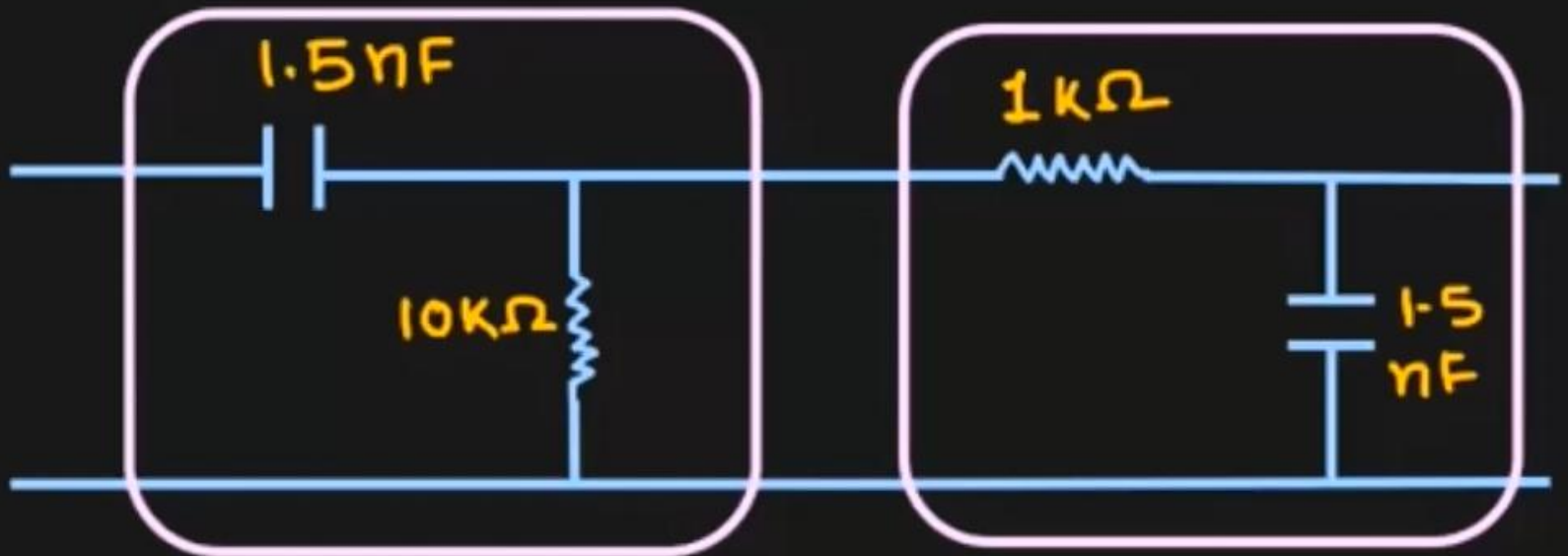

For High Pass Filter:

$$f_{C1} = \frac{1}{2\pi R C} = \frac{1}{2\pi \times (10K) \times (1.5nF)} = \underline{10.61KHz}$$

For Low Pass Filter:

$$f_{C2} = \frac{1}{2\pi RC} = \frac{1}{2\pi \times (1K) \times (1.5nF)} = 106.1KHz$$

Example


Find the bandwidth of the given Filter


$$f_{c1} = 10.61 \text{ kHz}$$

$$f_{c2} = 106.1 \text{ kHz}$$




Band Pass Filter

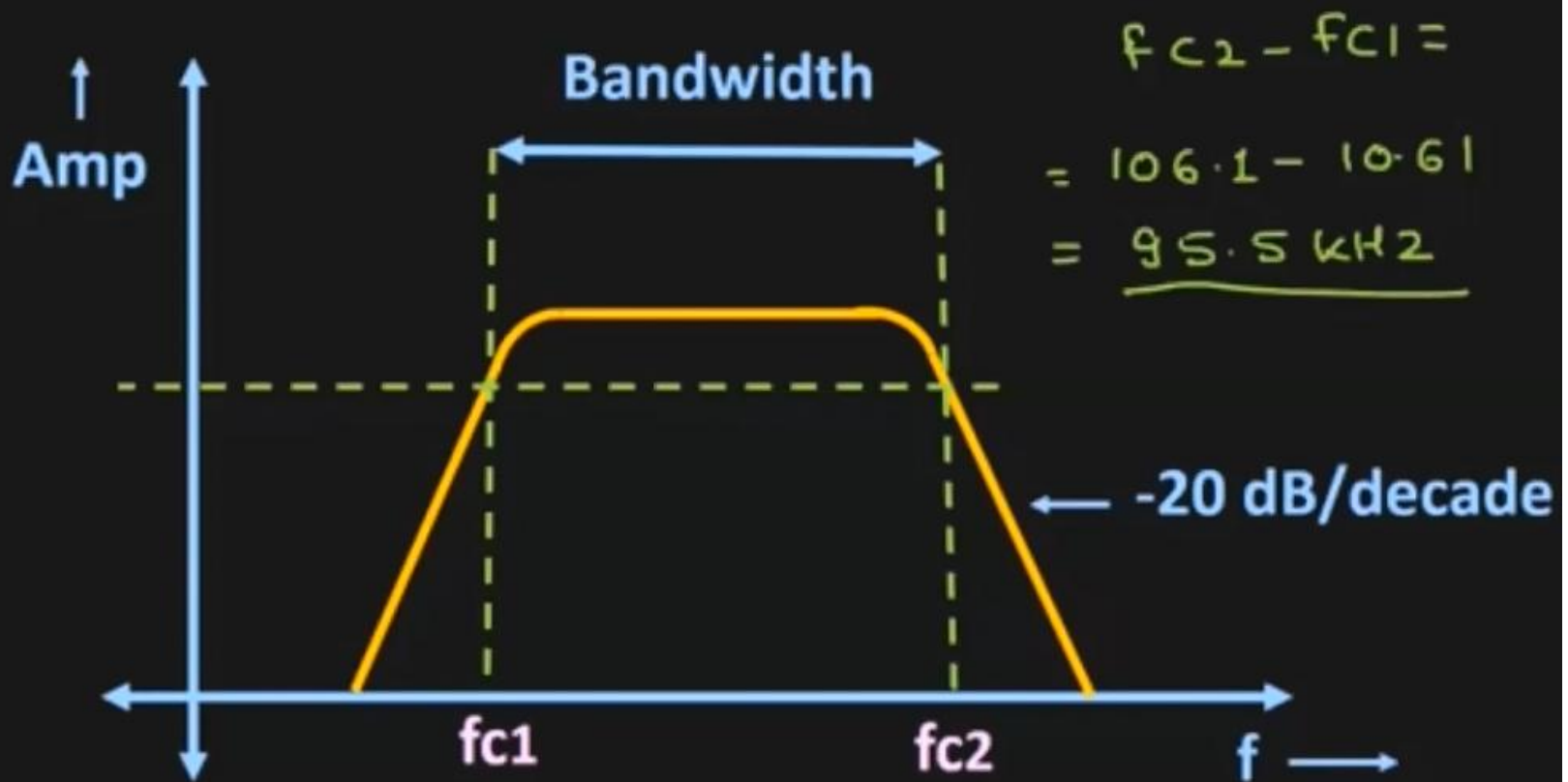

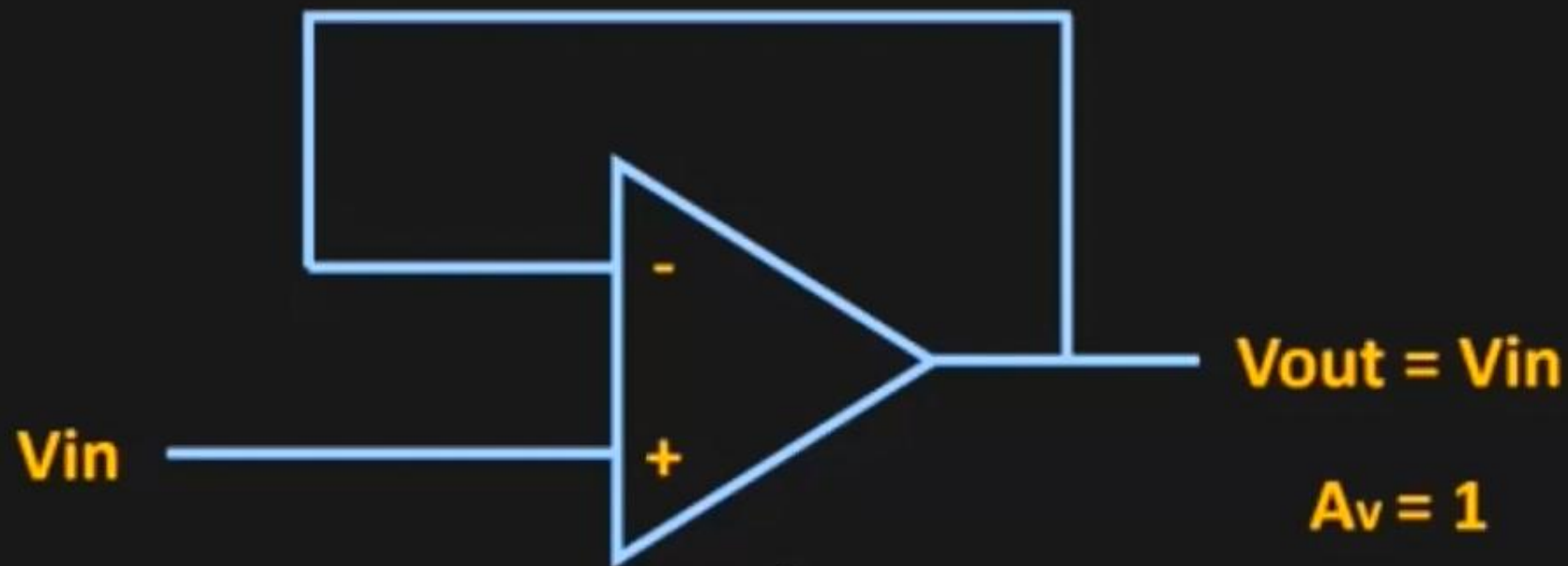


Op-amp as Voltage Follower


Active Band Pass Filter ($A_v=1$)

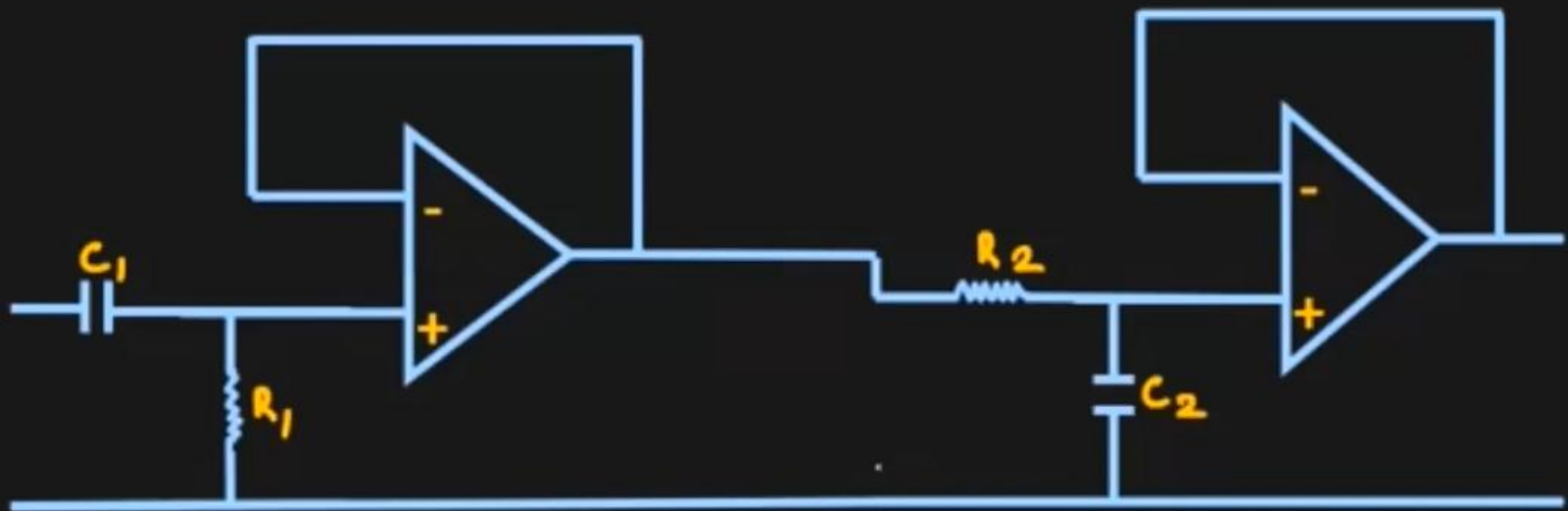


Band Stop Filter

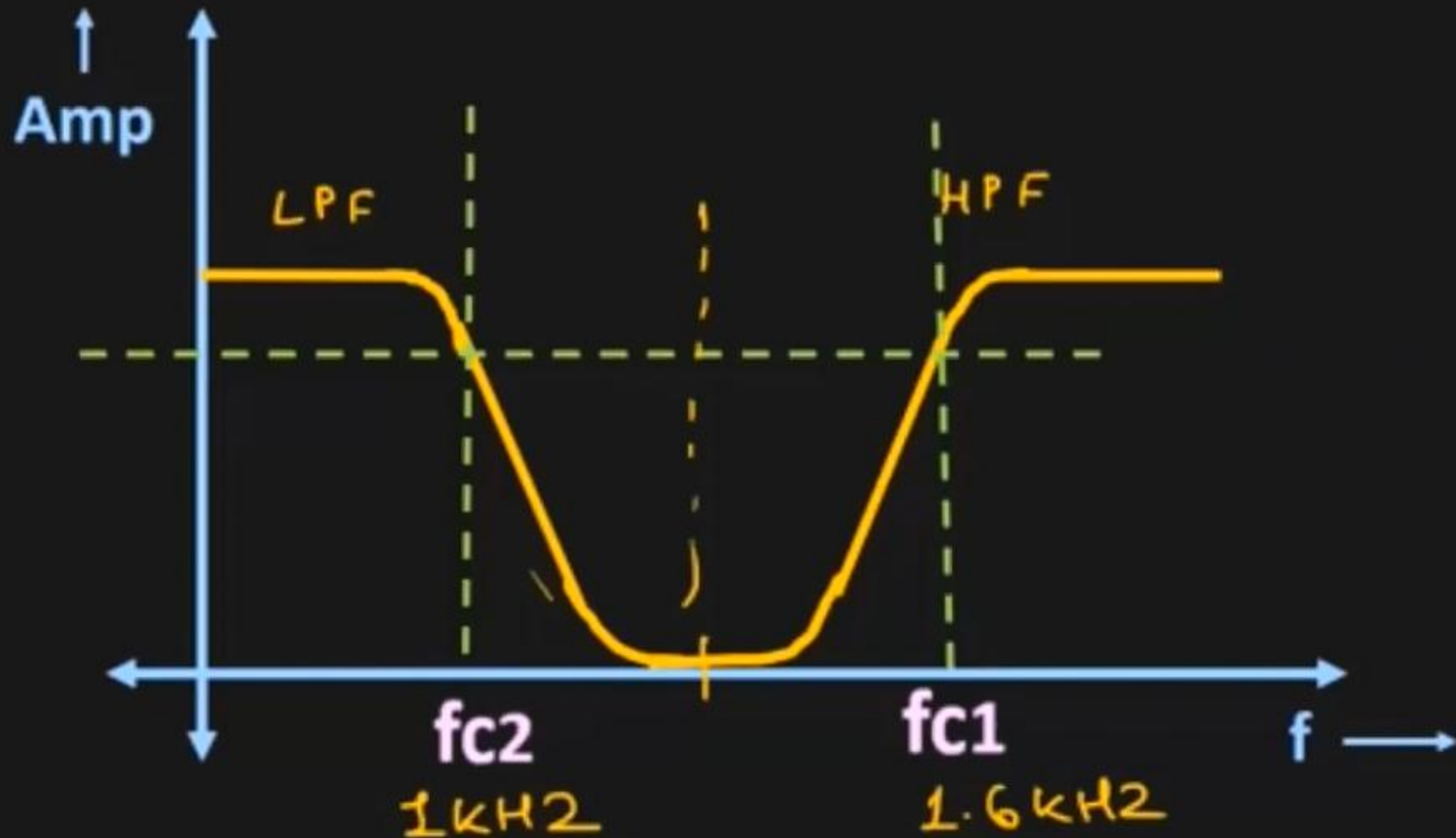


Parallel R-L-C Circuits

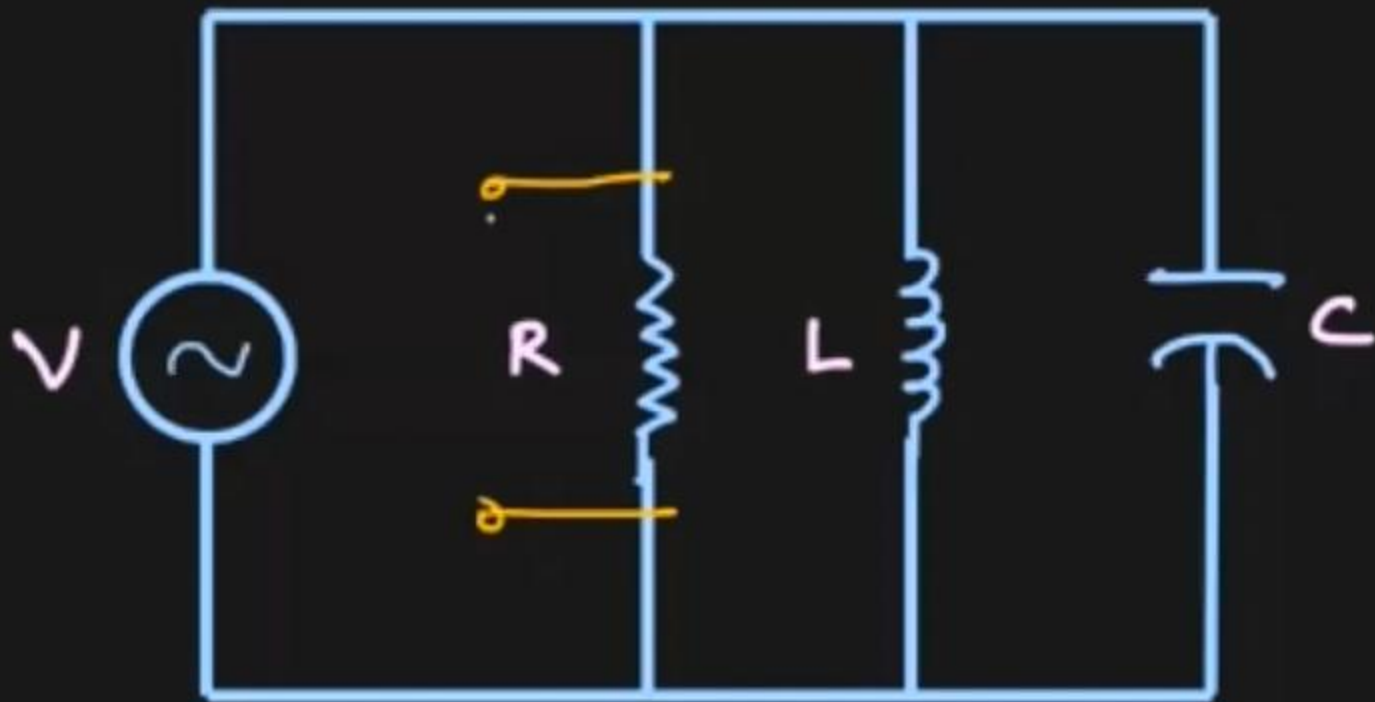


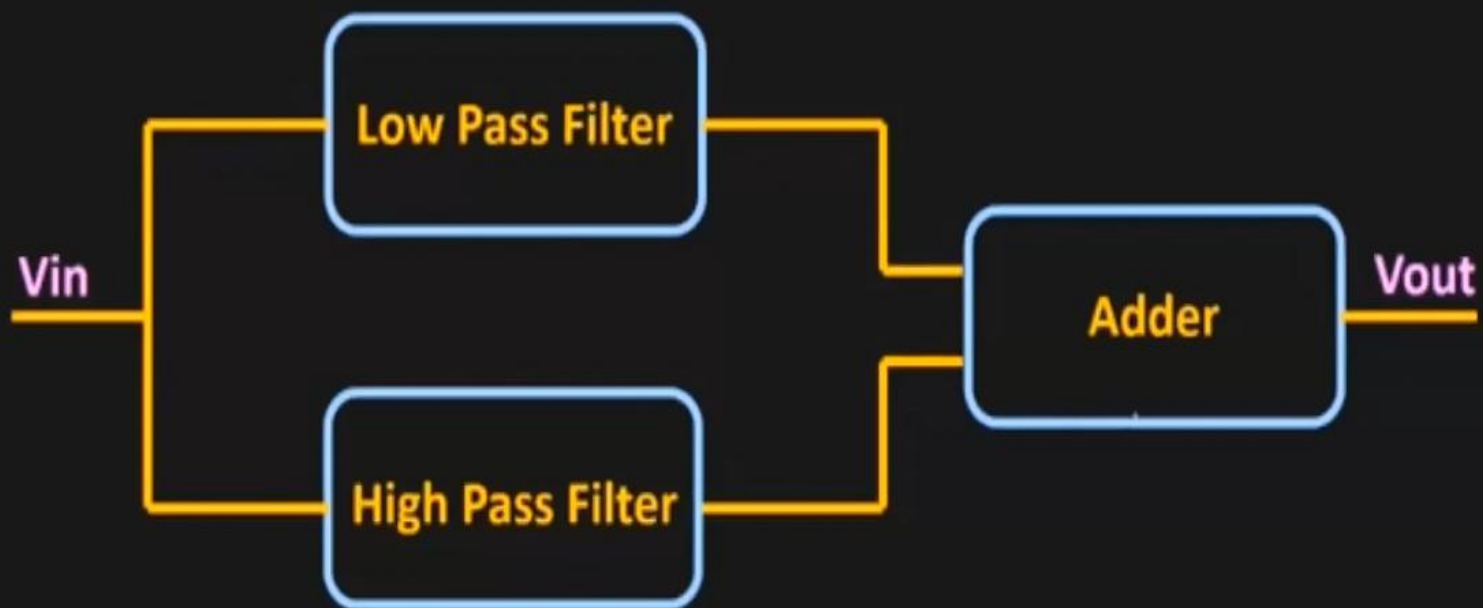

Band Stop Filter

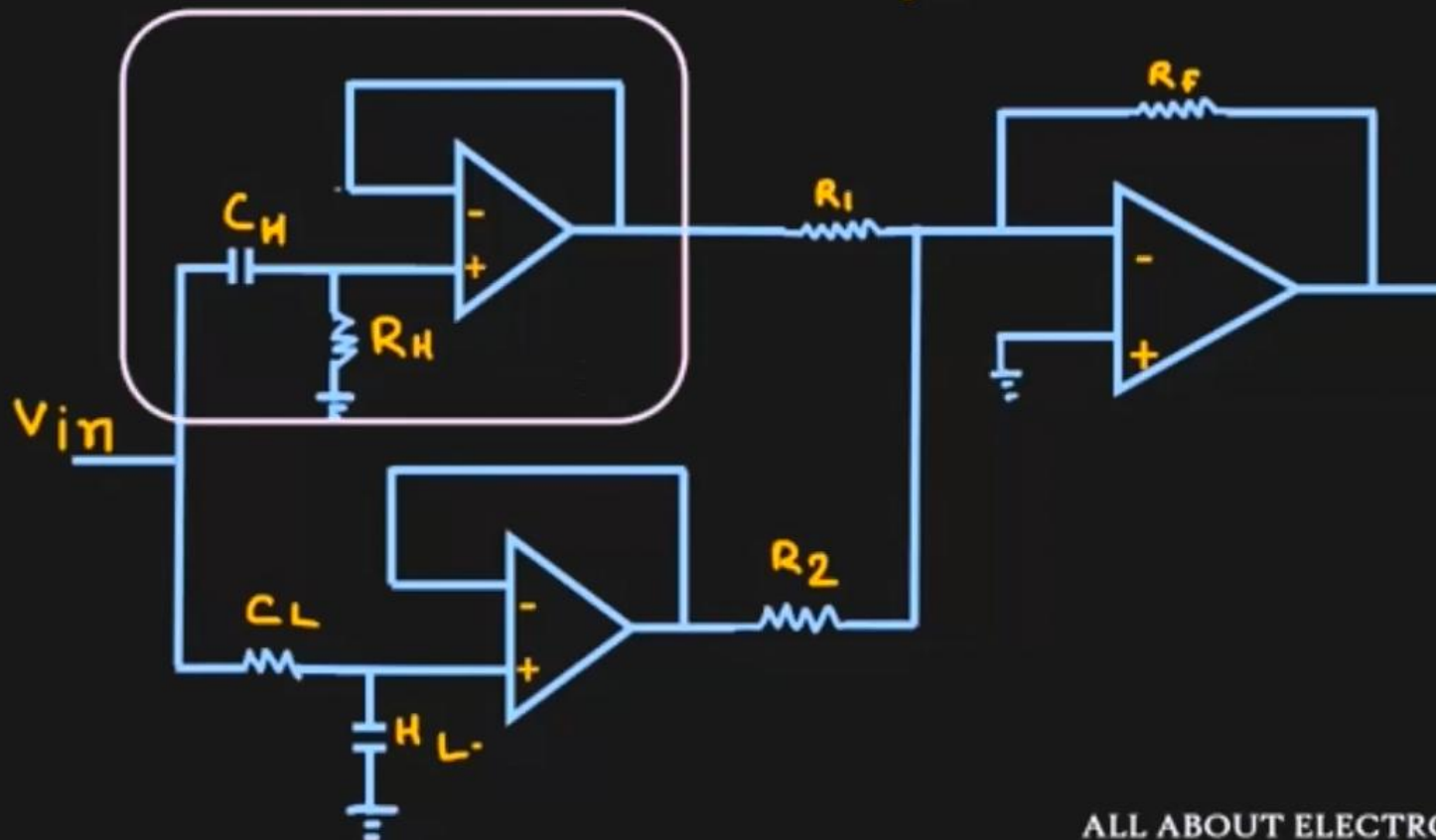


Band Stop Filter

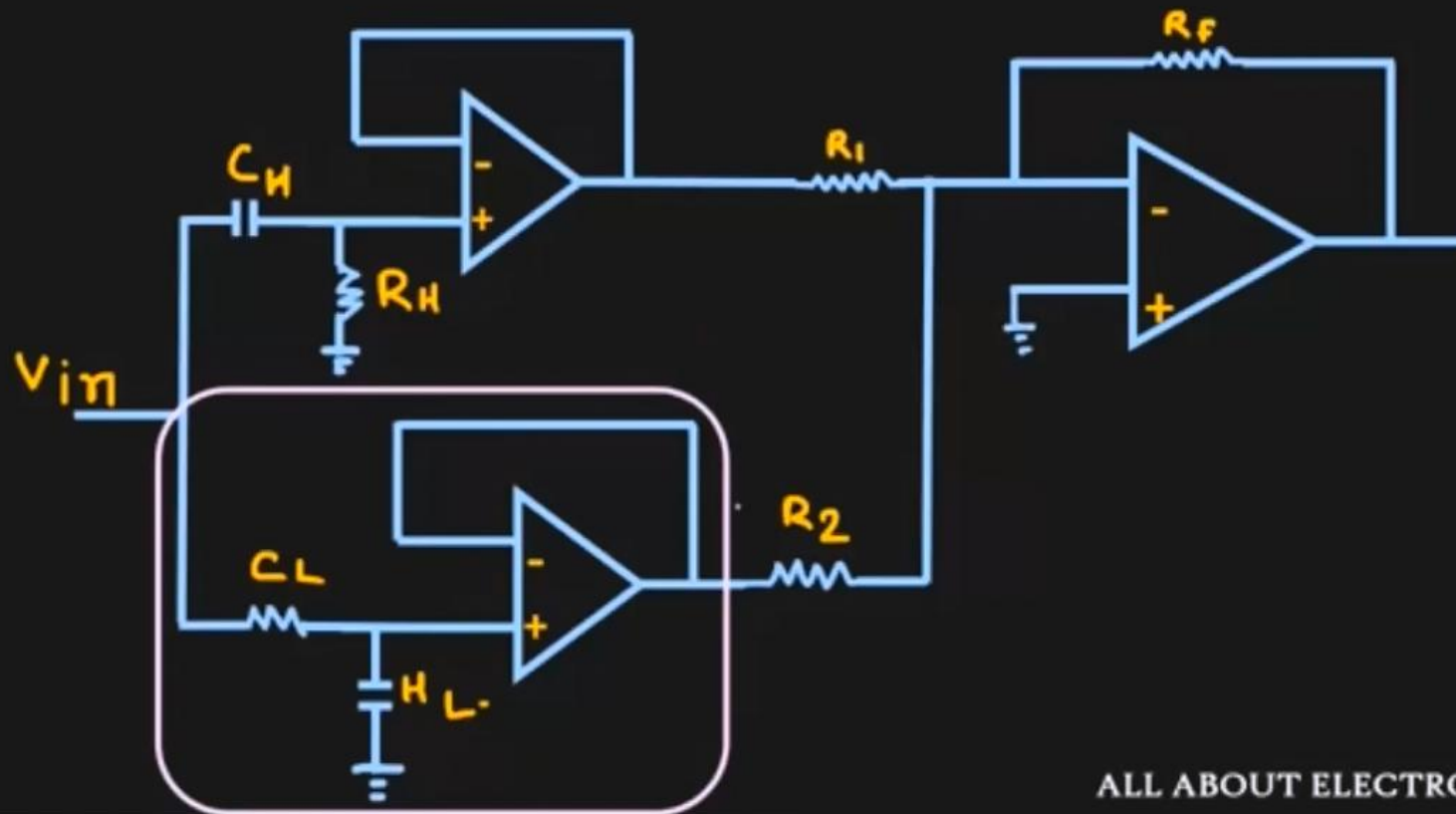

ALL ABOUT ELECTRONICS

Band Stop Filter

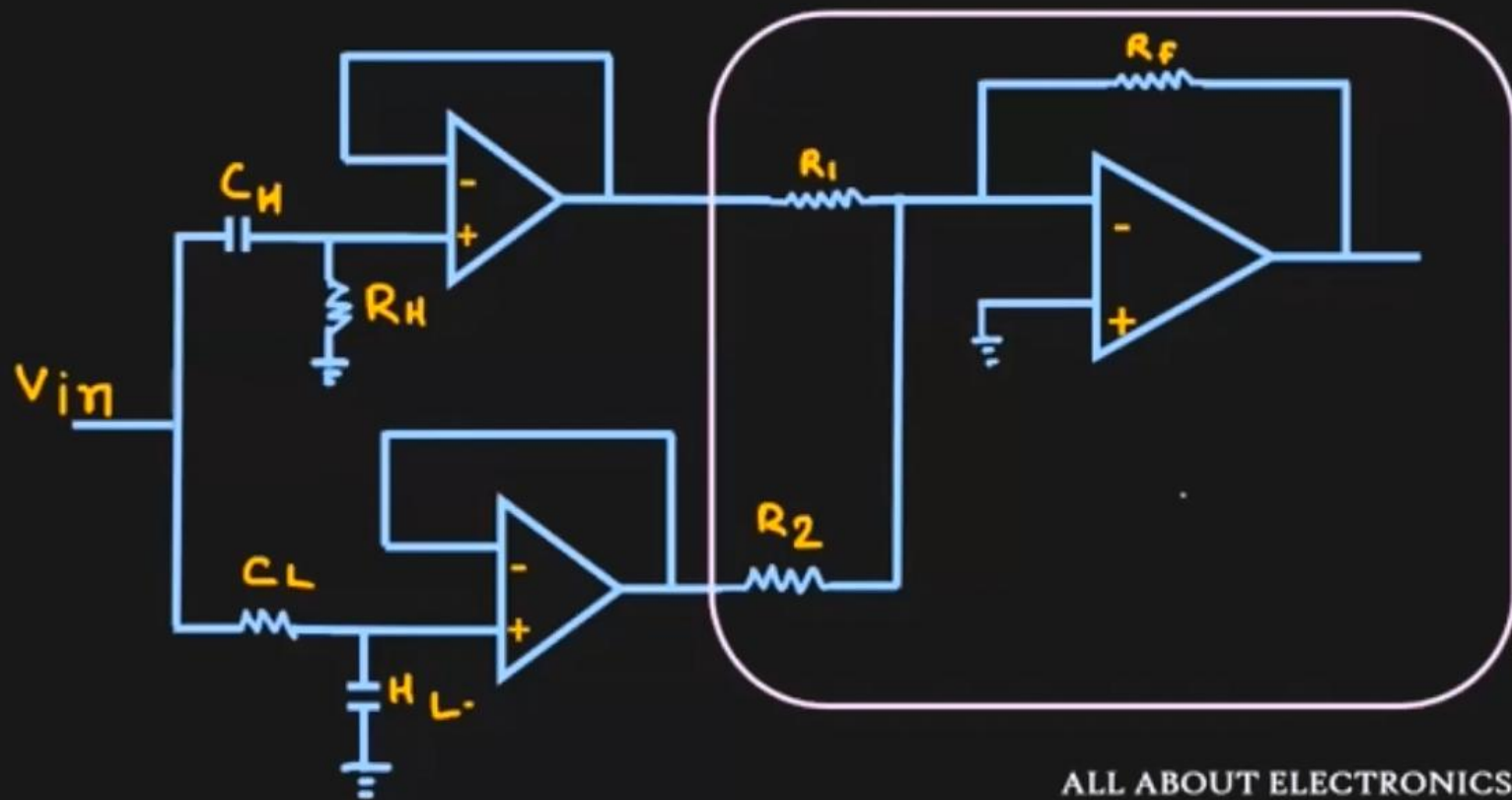

For High pass filter:


$$f_c = \frac{1}{2\pi \underline{R} \underline{C}} = \frac{1}{2\pi \times (10\text{K}) \times (0.01\mu\text{F})} = 1.59\text{KHz}$$


For High pass filter:

$$f_{C1} = \frac{1}{2\pi \underline{R} \underline{C}} = \frac{1}{2\pi \times (10\text{K}) \times (0.01\mu\text{F})} = \underline{1.59\text{KHz}}$$

For Low pass filter:
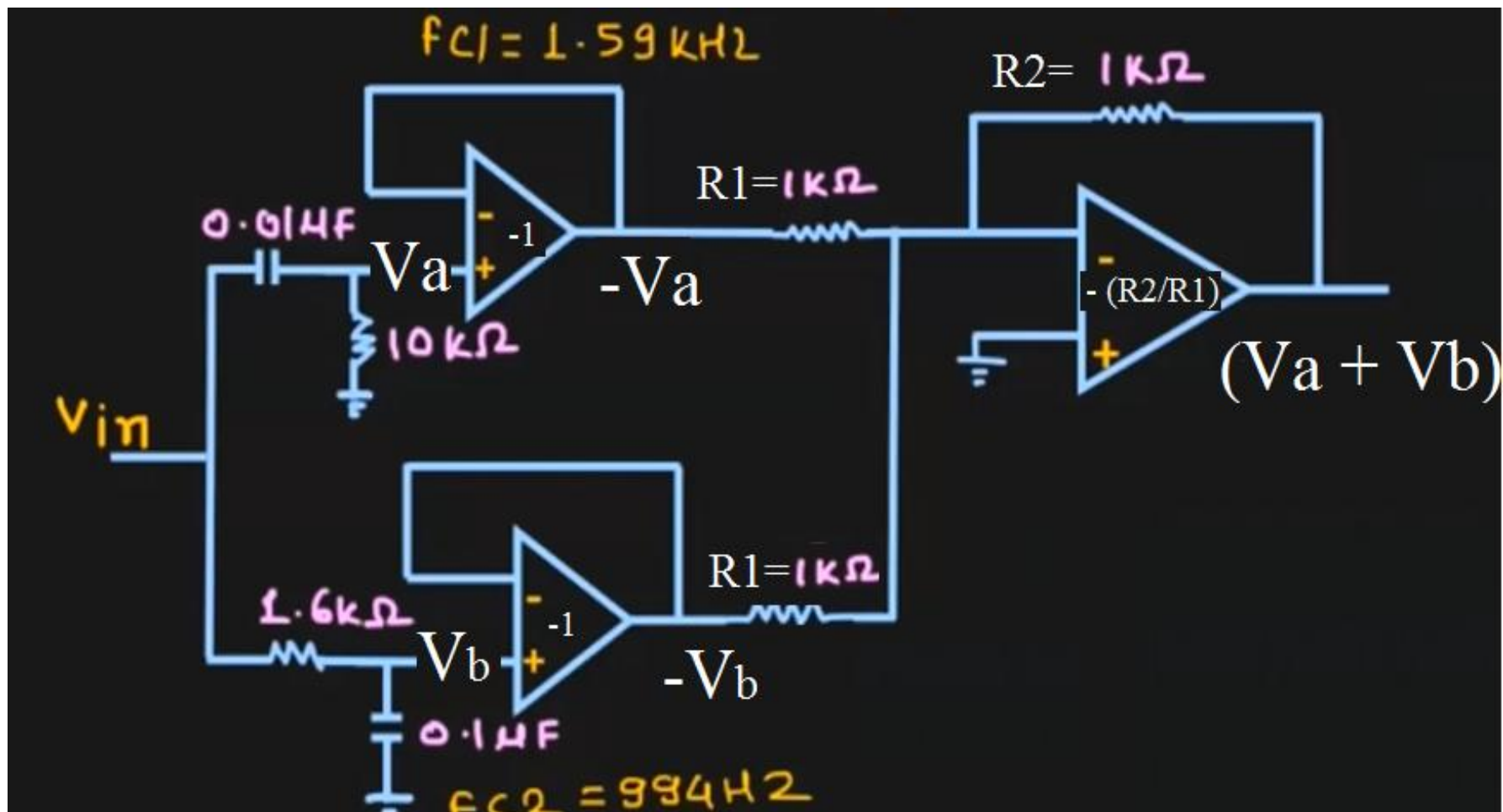
$$f_{C2} = \frac{1}{2\pi \underline{R} \underline{C}} = \frac{1}{2\pi \times (1.6\text{K}) \times (0.1\mu\text{F})} = 994\text{Hz}$$



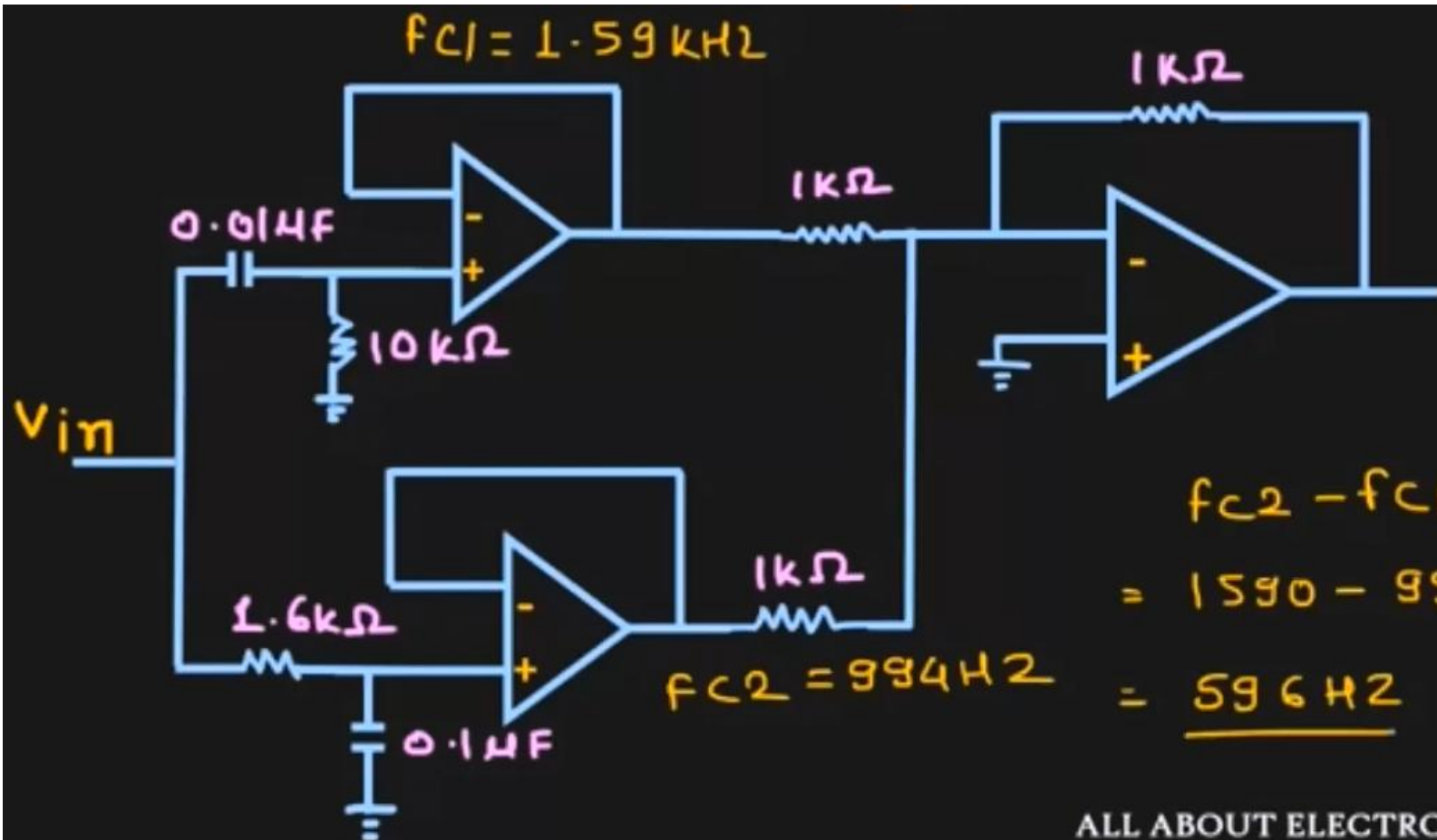

Band Stop Filter

